

165

**ISLAMIC UNIVERSITY OF TECHNOLOGY (IUT)**  
**ORGANISATION OF ISLAMIC COOPERATION (OIC)**

**Department of Computer Science and Engineering (CSE)**

**MID SEMESTER EXAMINATION**

**SUMMER SEMESTER, 2018-2019**

**DURATION: 1 Hour 30 Minutes**

**FULL MARKS: 75**

**CSE 4205: Digital Logic Design**

**Programmable calculators are not allowed. Do not write anything on the question paper.**

There are **4 (four)** questions. Answer any **3 (three)** of them.

Figures in the right margin indicate marks.

1. a) Convert the followings: 2.5x4
  - i.  $(41.687)_{10} = (?)_2$
  - ii.  $(DADA.B)_{16} = (?)_{10}$
  - iii.  $(153.513)_{10} = (?)_8$
  - iv.  $(198)_{12} = (?)_{10}$

**Hints:** Calculate maximum upto 3 digits after the decimal point where necessary. You have to show the procedures, only values produced by the calculator will not suffice.
- b) Describe odd parity and even parity with example. 5
- c) i. What is radix complement and diminished radix complement? 2+4+4  
 ii. By r's complement perform:  $(-9286)_{10} + (+801)_{10} = (?)_{10}$   
 iii. By (r-1)'s complement perform:  $(1000100)_2 - (1010100)_2 = (?)_2$
2. a) What is parity bit? Define odd parity and even parity with examples. 1+2+2  
 b) Define BCD. Perform addition after converting the values into BCD:  $(791)_{10} + (658)_{10} = (?)_{10}$  1+4  
 c) Simplify the boolean expression using K-map for - 15  
 $\sum m(0,4,6,8,12,13,14,15,16,17,18,21,24,25,26,28,29,31)$
3. a) Define followings with example: 2x5
  - i. Grey Code
  - ii. Checker Board Pattern
  - iii. Product of Sum
  - iv. Sum of Product
  - v. Universal Gate
- b) Draw the circuits and write the boolean expressions for the following gates using nand gate: 2x6
  - i. AND
  - ii. OR
  - iii. XOR

Repeat the instruction for i-iii but this time using nor gate.
- c) What will be the simplified boolean expression for this K-map? 1+2  
 Prove the expression using a truth table.

	00	01	11	10
0	0	1	0	1
1	1	0	1	0

Figure 1: K-map

4. a) Define combinatorial & sequential circuit with example. 1.5x2  
 b) What is full adder? For sum and carry of a 1-bit full adder, give boolean expression, truth table and circuit diagram. 1+6  
 c) Simplify the boolean expression using Tabular method for  $\sum m(2,3,4,5,6,7,9,13,15)$  15