

ISLAMIC UNIVERSITY OF TECHNOLOGY (IUT)
ORGANISATION OF ISLAMIC COOPERATION (OIC)

DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING

Semester Final Examination
Course No.: Phy 4241
Course Title: Physics II

Summer Semester, A. Y. 2017-2018

Time: 3 Hours

Full Marks: 150

There are 8 (eight) questions. Answer any 6 (six) questions. All questions carry equal marks. Marks in the margin indicate full marks. Programmable calculators are not allowed. Do not write on this question paper.

1. a) The circuit of Fig. 1(a) contains five identical capacitors. Find the value of C .

09

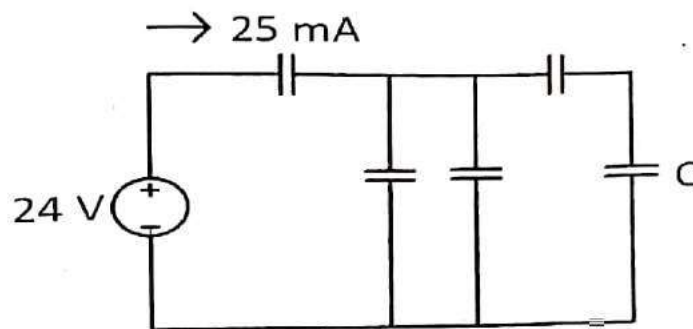


Fig. 1(a)

- b) Determine L_{eq} of the inductive network of Fig. 1(b) at the terminals a-b.

13

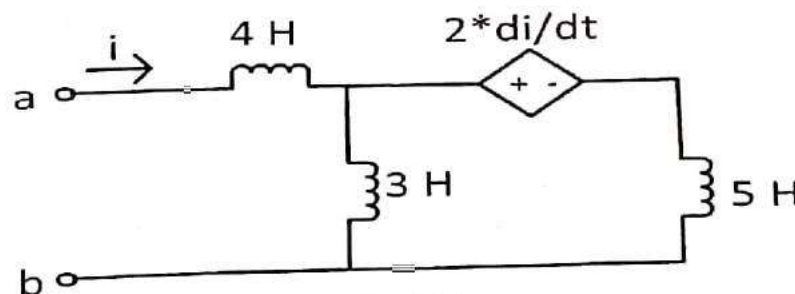


Fig. 1(b)

- c) The current through a 12 mH inductor is $4 \sin(100t)$ A. Find the voltage across the inductor for $0 < t < \frac{\pi}{200}$ s and the energy stored at $t = \frac{\pi}{200}$ s.

03

2. a) Calculate the mesh currents, I_1 and I_2 in the circuit of Fig. 2(a)

10

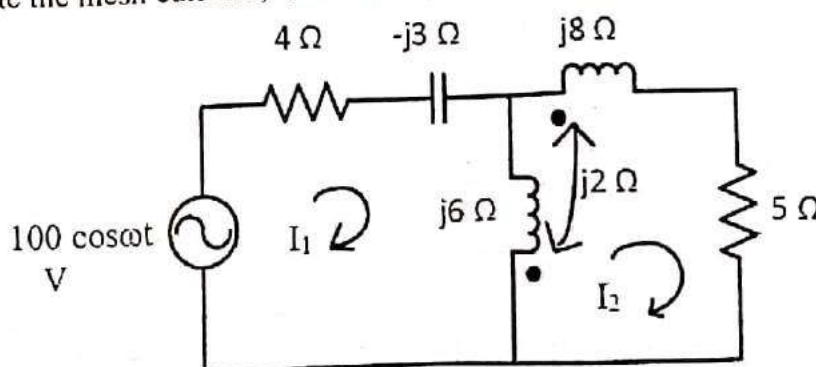


Fig. 2(a)

b) For the network in Fig. 2(b), find Z_{ab} and I_0 .

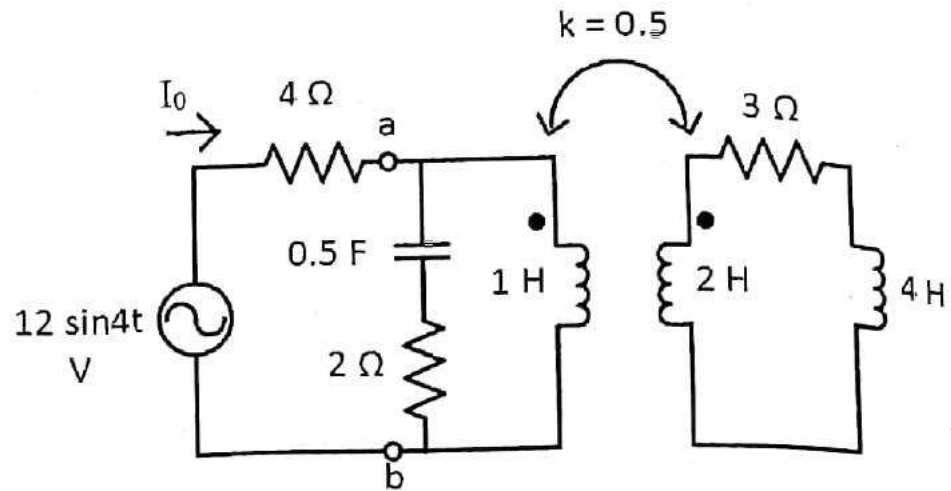


Fig. 2(b)

3. a) Find the current, I in the circuit of Fig. 3(a).

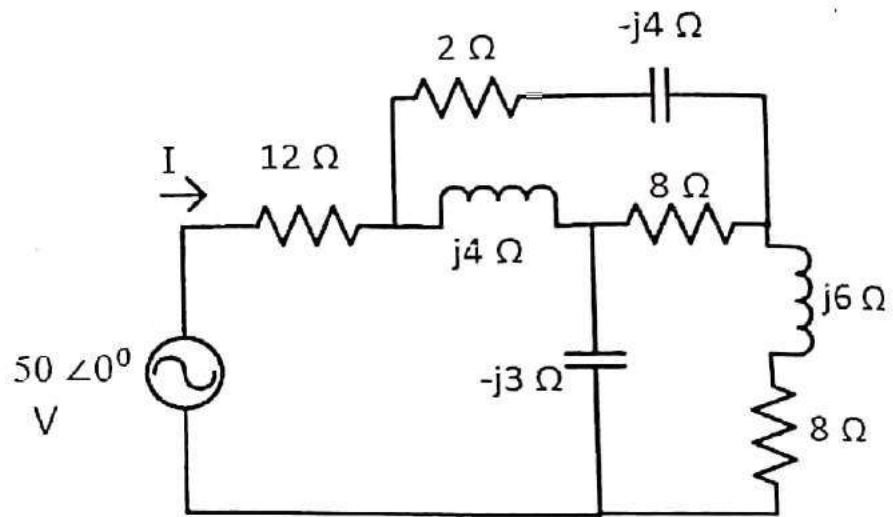


Fig. 3(a)

b) In the circuit of Fig. 3(b), find V_s if $I = 2 \angle 0^\circ$ A.

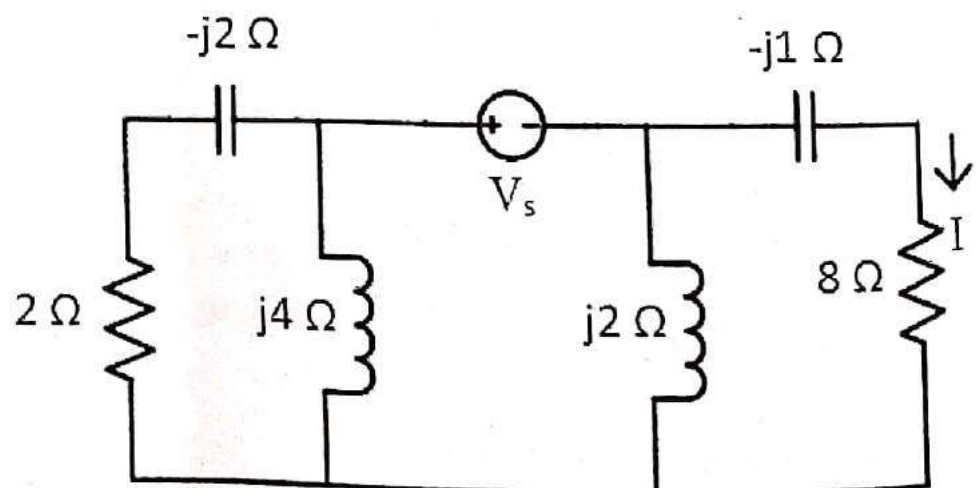


Fig. 3(b)

4. a) In solving for currents using mesh analysis, the following equations are obtained. Draw the circuit and find the currents. 12
- $$\begin{aligned} 15 i_1 - 10 i_2 &= -10 \\ 10 i_1 - 22 i_2 + 10 i_3 &= 0 \\ 10 i_2 - 15 i_3 &= 12 \end{aligned}$$
- b) Find the current, i in the $10 \text{ k}\Omega$ resistor in the circuit shown in Fig. 4(b) by making a succession of appropriate source transformations. 13

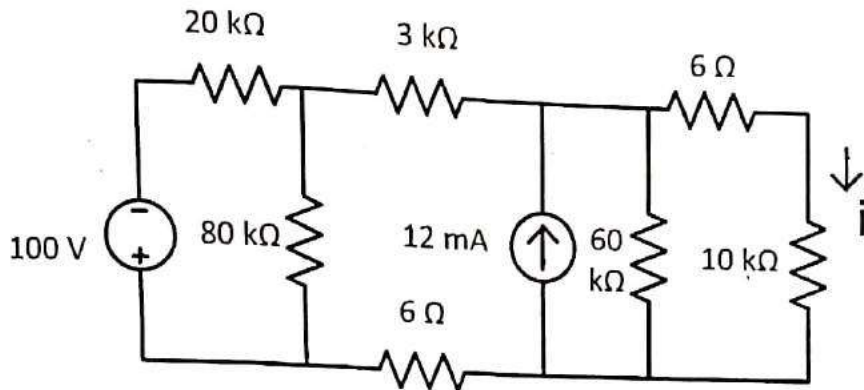


Fig. 4(b)

5. a) Find the average power absorbed by the 8Ω resistor in the circuit shown in Fig. 5(a). 18

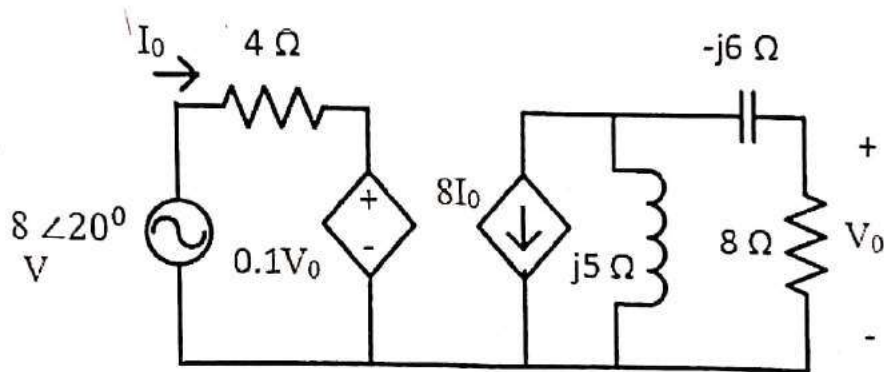


Fig. 5(a)

- b) Determine the Thevenin equivalent of the circuit in fig. 5(b) as seen from the terminals a-b. 07

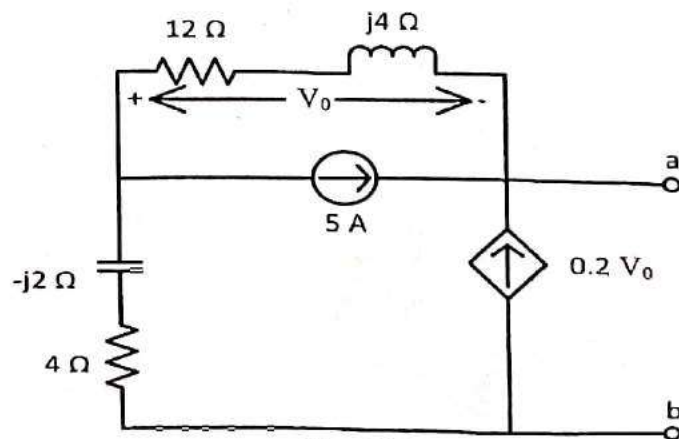


Fig. 5(b)

6. a) Obtain the inductor current, $i(t)$ for both $t < 0$ and $t > 0$ in the circuit of Fig. 6(a).

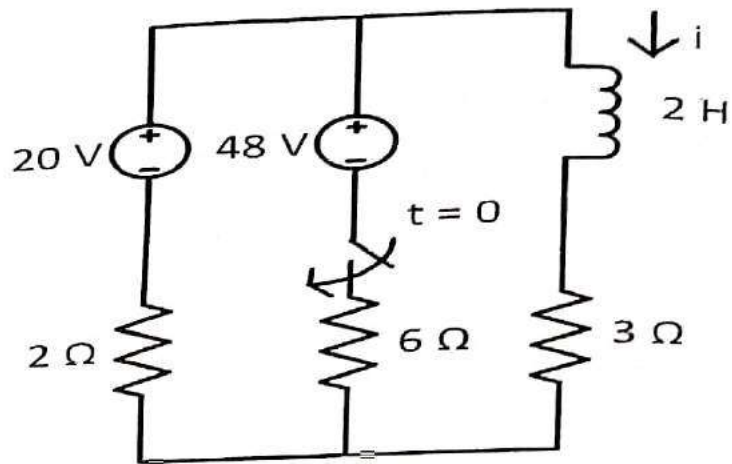


Fig. 6(a)

- b) Find the current, $i(t)$ for both $t < 0$ and $t > 0$ in the circuit shown in Fig. 6(b).

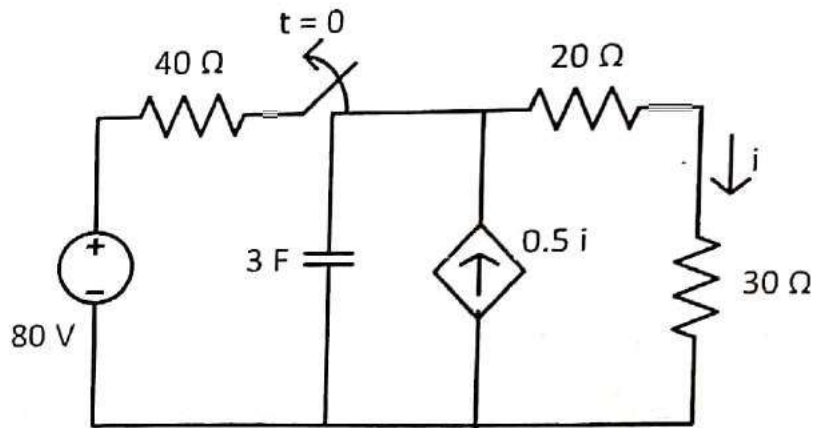


Fig. 6(b)

7. a) Compute the value of R that results in maximum power transfer to the $10\ \Omega$ resistor shown in Fig. 7(a). Find the maximum power.

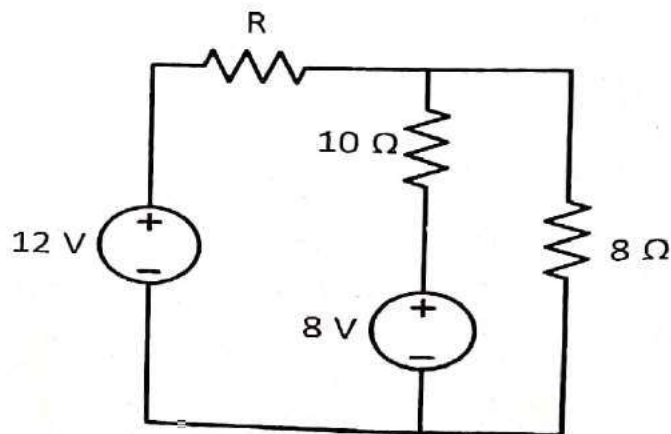


Fig. 7(a)

- b) Obtain the Norton equivalent of the circuit shown in Fig. 7(b) to the left of terminals x-y. Use the result to find the current, i .

15

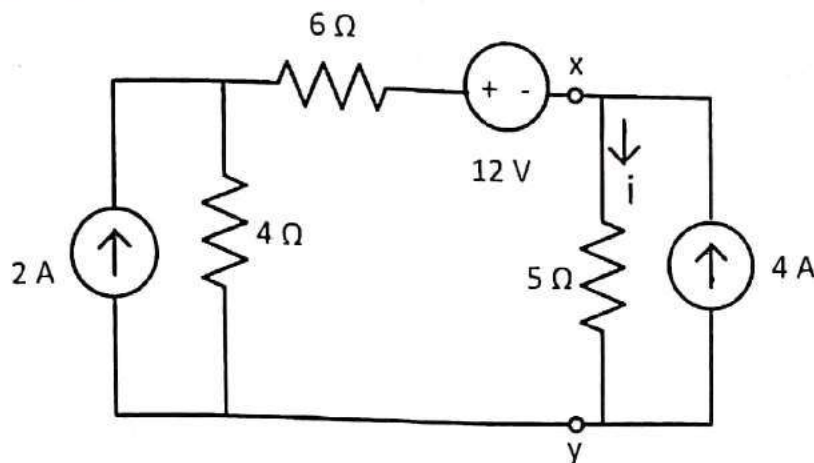


Fig. 7(b)

8. a) Select values for R_1 and R_2 in the circuit of Fig. 8(a) so that $V_R(0^+) = 10$ V and $V_R(1 \text{ ms}) = 5$ V.

12

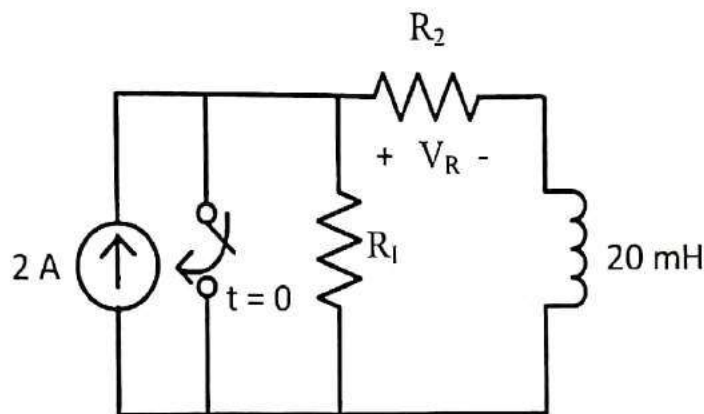


Fig. 8(a)

- b) For the circuit shown in Fig. 8(b), Find equivalent resistance by looking into terminals a-b. For finding equivalent resistance, connect a 1 A current source across terminals a-b. (No other method will be acceptable).

13

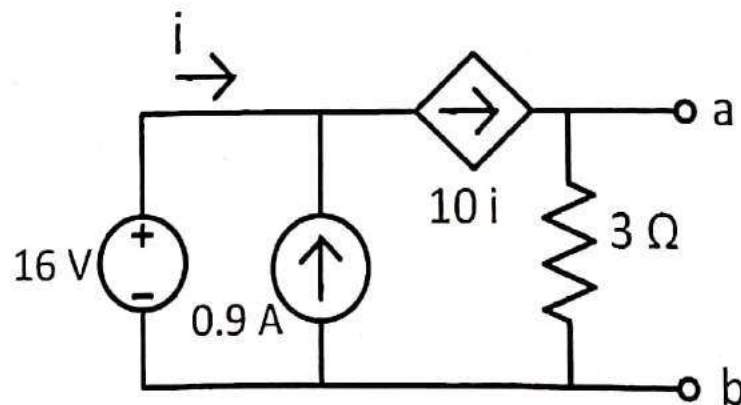


Fig. 8(b)