

ISLAMIC UNIVERSITY OF TECHNOLOGY (IUT)
ORGANISATION OF ISLAMIC COOPERATION (OIC)

DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING

Mid-Semester Examination

Course No.: Phy 4241

Course Title: Physics II

Summer Semester, A.Y. 2015-2016

Time: 90 Minutes

Full Marks: 75

There are 4 (four) questions. Answer any 3 (three) questions. All questions carry equal marks. Marks in the margin indicate full marks. Programmable calculators are not allowed. Do not write on this question paper.

1. a) Find the equivalent resistance with respect to terminals A and B in the circuit of Fig. 1(a). Assume all the resistance values are equal to $1\text{ k}\Omega$. 15

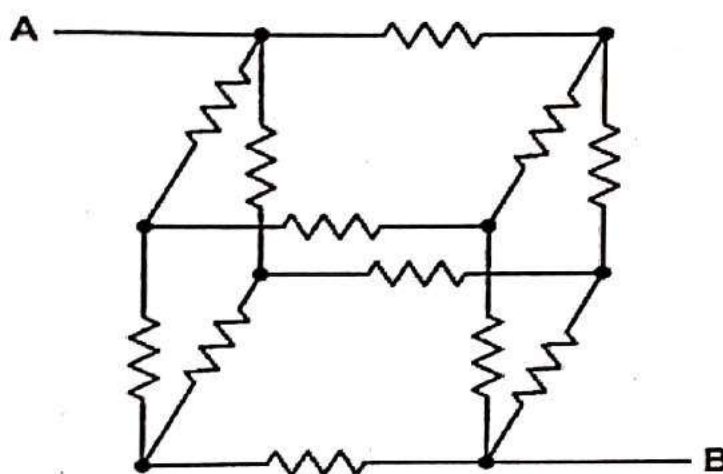


Fig. 1(a)

- b) Assume a current of 3 ampere is entering through the terminal A in the circuit of Fig. 1(a). Now determine all the branch currents and show them in a diagram. 10
2. a) Calculate the value of I_1 from the circuit in Fig. 2(a). 15

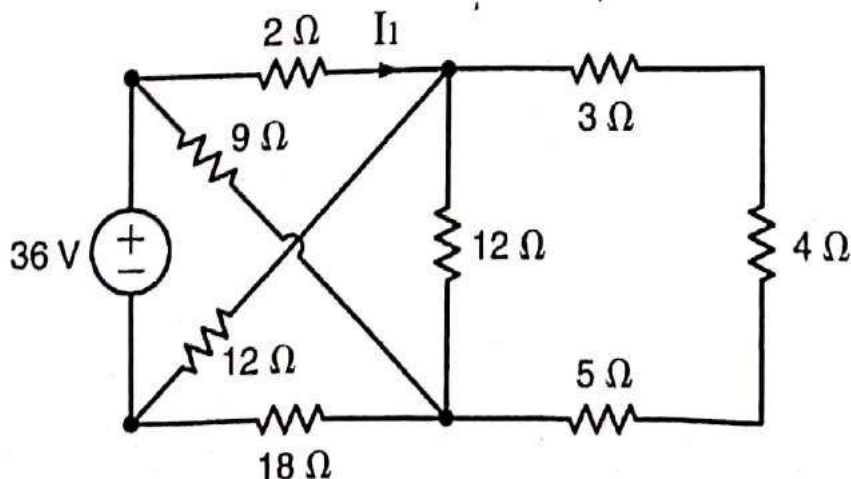


Fig. 2(a)

- b) State the maximum power transfer theorem. For a circuit with ideal source, derive the condition for maximum power transfer with power vs. load graph. 10

3. a) Use mesh analysis to obtain i_o in the circuit of Fig. 3(a).

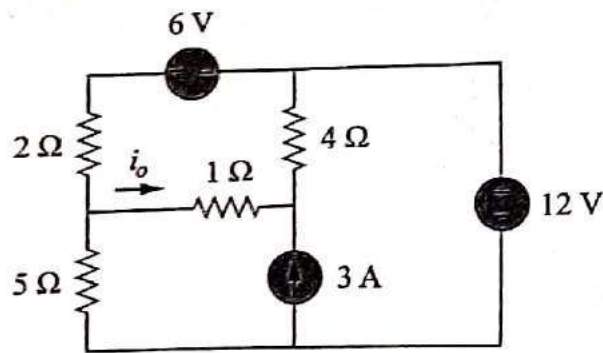


Fig. 3(a)

- b) Derive the equations to convert a delta connected resistance network to an equivalent wye connected resistance network and vice-versa.

4. a) Find out all the node voltages in the circuit of Fig. 4(a).

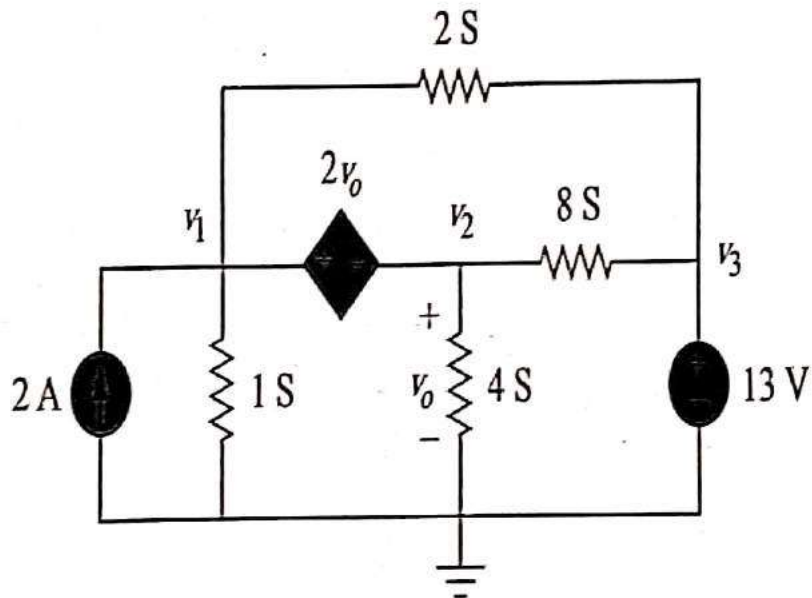


Fig. 4(a)

- b) Determine the value of R_L when maximum power is transferred in R_L in the circuit of Fig. 4(b). What is the maximum power?

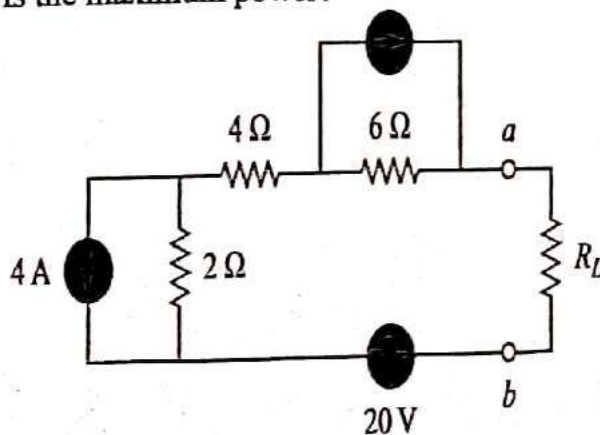


Fig. 4(b)